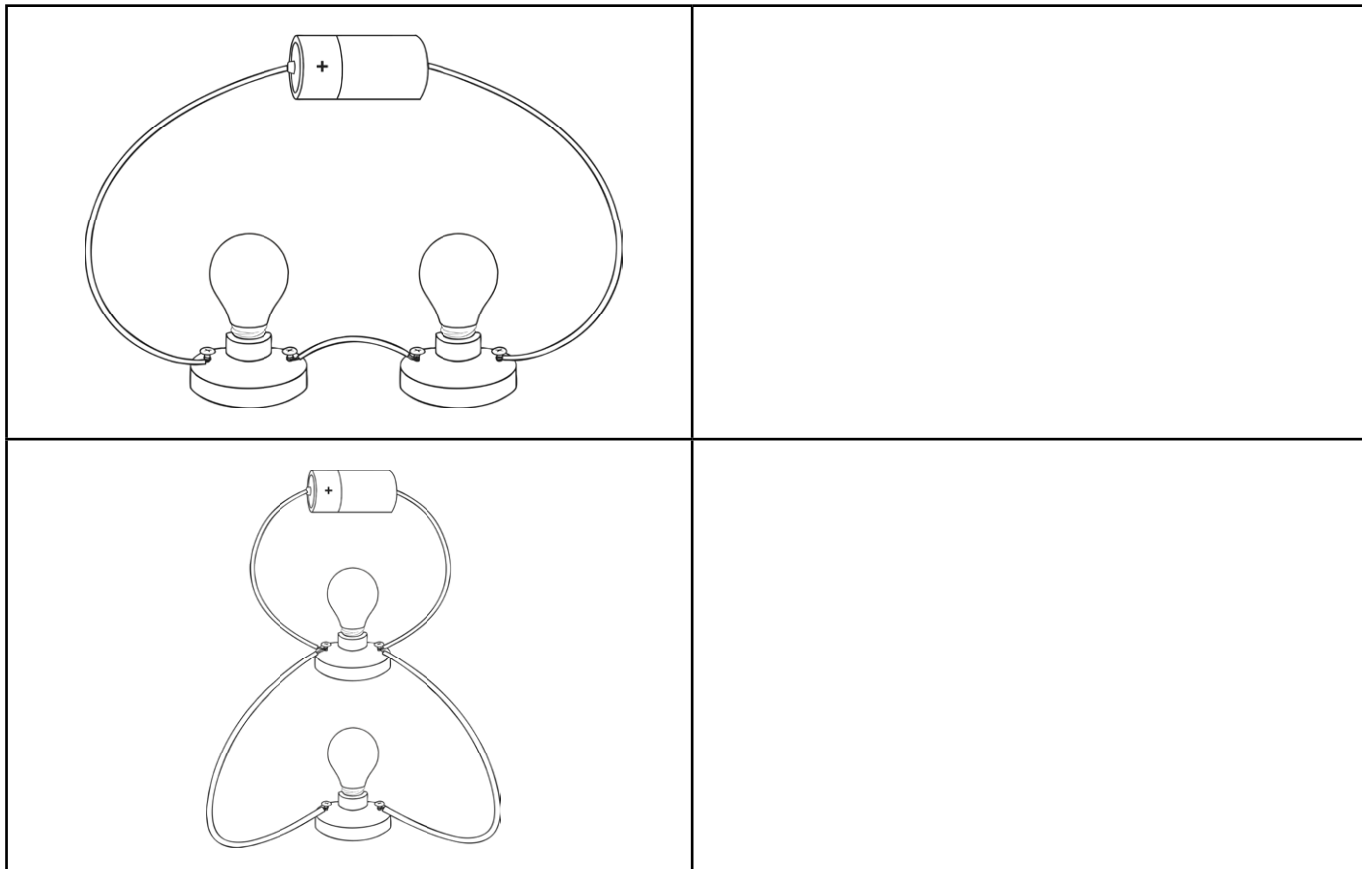


Circuits



Make both of these circuits.

Re-draw the series and parallel circuit using the symbols.




lamp



motor



battery

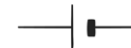

switch



buzzer

